

# LAB 9 - OHM'S LAW & BULBS

PHYS 112

ISAAC WOODARD


OCTOBER 27, 2020

# OHM'S LAW: EQUATION 1

$$R = \frac{\Delta V}{I}$$

# RESISTORS IN SERIES: EQUATION 2


$$R_{eq} = R_1 + R_2 + \dots$$

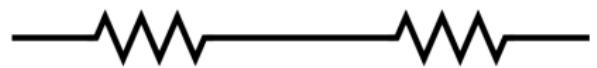

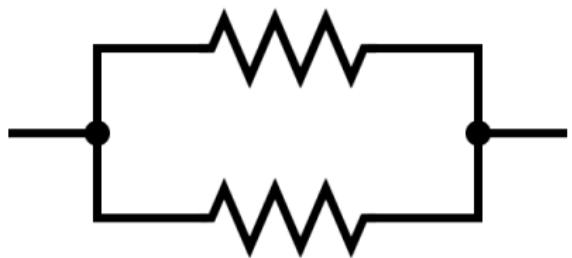
# RESISTORS IN PARALLEL: EQUATION 3

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$


$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$





# COMPLEX CIRCUIT

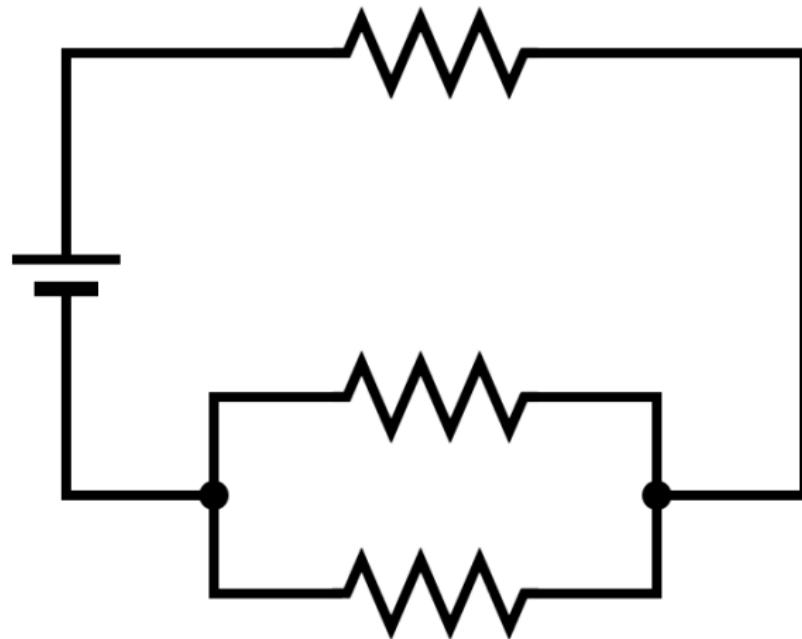

# EQUIPMENT SETUP

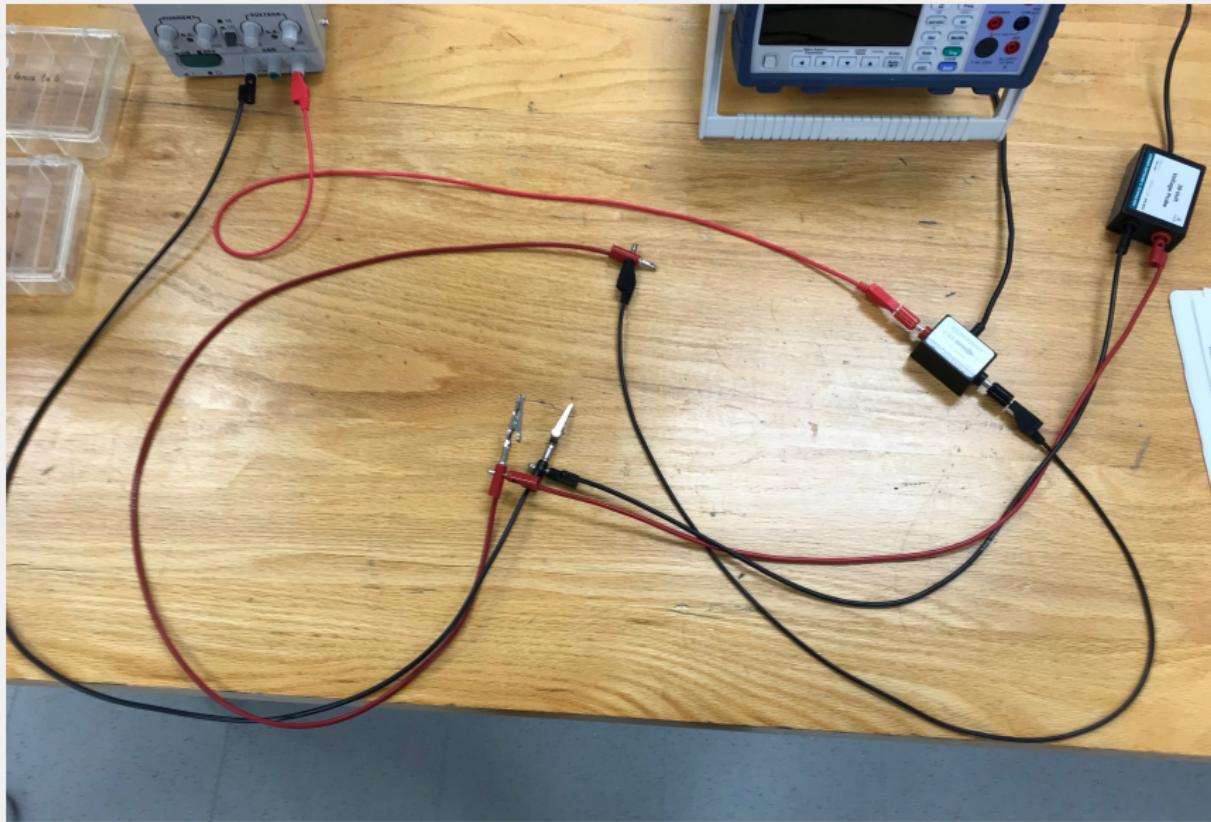

# SCHEMATIC SYMBOLS

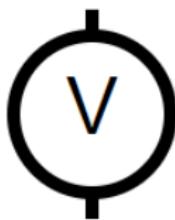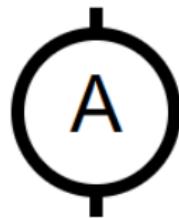

# SCHEMATIC EXAMPLE

